

- $V_j \approx 1V$ (pointes importantes)

D'après fiche technique :

$$U_2 = 14,8V ; I_2 = 50mA ; r_2 = 5\Omega$$

$$P_{max} = 1W$$


$$- U_{Z_0} = U_2 - r_2 I_2 = 14,8 - 5 \cdot 50 = 14,55V$$

$$- U_{C,max} = \sqrt{2} (U_1 - 2V_j) = \sqrt{2} \cdot 18 - 2 \cdot 1 \\ = 23,46V$$

$$- U_{C,min} = U_{C,max} + (U_{Z_0} - U_{C,max}) (1 - \exp \left(- \frac{0,4T_0}{C(R_s + r_2)} \right))$$

$$= 23,66 + (-14,55 - 23,66) (1 - \exp \left(- \frac{8ms}{22ms} \right))$$

$$U_{C,min} = 20,74V$$

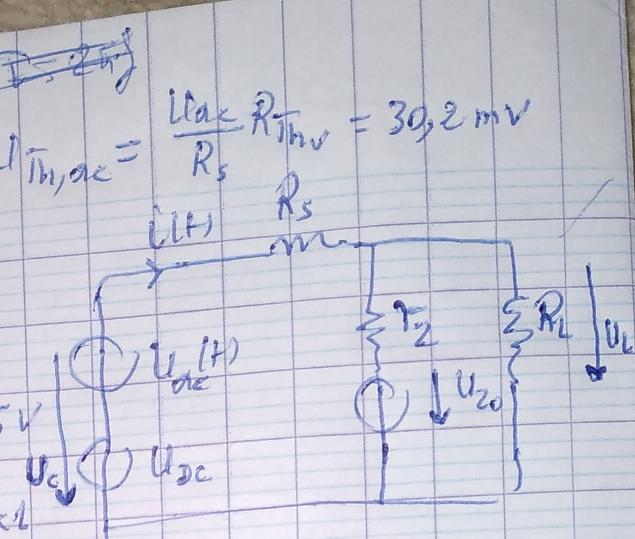

$$- \Delta U_C = U_{C,max} - U_{C,min} = 2,72V$$

$$- U_{C,dc} \approx U_{C,max} - \frac{\Delta U_C}{2}$$

$$= 23,46 - \frac{2,72}{2} = 22,18$$

$$- U_{L,dc} = U_{Th,dc} \frac{R_L}{R_{Th,dc} + R_L} = 14,65V$$

$$- U_{L,dc} = U_{Th,dc} \frac{R_L}{R_{Th,dc} + R_L} = 30mV$$

- Ondulation relative

$$U_{C,dc} = \frac{\Delta U_C}{2} = \frac{2,72}{2} = 1,36V$$

$$\frac{U_{L,dc}}{U_{L,dc}} = \frac{30mV}{14,65V} = 0,2\%$$

$$- R_{Th} = \frac{R_s r_2}{R_s + r_2} = 1,89\Omega$$

- Puissance moyenne fournie à la charge :

$$- U_{Th,dc} = \left(\frac{U_{dc}}{R_s} + \frac{U_{Z_0}}{r_2} \right) R_{Th,dc} = 14,72V \quad P_{L,dc} = \frac{U_{L,dc}^2}{R_L} \approx 0,2W$$

$$I_{Z,\max} = \frac{U_{L,\max} - U_{Z_0}}{R_2}$$

$$\approx \frac{U_{L,dc} + U_{L,ac} - U_{Z_0}}{R_2} = 25 \text{ mA}$$

$$I_{Z,\min} = \frac{U_{L,\min} - U_{Z_0}}{R_2}$$

$$\approx \frac{U_{L,dc} - U_{L,ac} - U_{Z_0}}{R_2} = 13 \text{ mA}$$

$$P_{Z,\text{moy}} = U_{Z,\text{moy}} I_{Z,\text{moy}} = U_{L,dc} I_{Z,\text{moy}}$$

$$= U_{L,dc} \frac{I_{Z,\max} + I_{Z,\min}}{2} = 0,3 \text{ W}$$

$$I_{DC} = I_Z + I_L = \frac{U_{L,dc} - U_{Z_0}}{R_2} + \frac{U_{L,dc}}{R_L}$$

$$(I_{DC} = 34 \text{ mA})$$

$$I_{C,\max} = 2 I_{DC} \frac{T - dt}{Dt}$$

$$= 2 I_{DC} \frac{0,8T}{92T} = 8 I_{DC}$$

$$\approx 270 \text{ mA}$$